

## Documentation for Lab 5 part 5 New Additions

### **bne – Branch Not Equal**

This instruction moves the PC by a given amount if the given registers do not hold equal values.

Instruction Structure : bne 0x(immediate\_value) (register1) (register2)

example : bne 0x02 1 2

opcode : 0000\_1000

changes : bne was implemented just like beq, a new CU signal was introduced and it was high for bne, according to the opcode. Inverse of the ALUZERO signal was taken and from that and the new CU signal, PC was changed using the value extracted from Immediate value.

## srl – Logical Shift Right

This instruction right shifts a value in a specified register by the amount specified in the immediate value, and stores in a specified register.

Instruction Structure : srl (store reg) (value taken reg) 0x(immediate\_value)


example : srl 4 1 0x02

take the value in reg1 right shift it by 2 bits and store it in reg4

opcode : 0000\_1001

changes : a new module was added to the ALU and it has 24 muxes. A new ALU opcode was introduced and it is selected in the CU when necessary.  
Mux diagram is shown below.

 Timing : to simulate the delays, 2 time units of delay was added to the new module inside ALU



8-bit logical right shifter.

## sll – Logical Shift Left

This instruction left shifts a value in a specified register by the amount specified in the immediate value, and stores in a specified register.


Instruction Structure : sll (store reg) (value taken reg) 0x(immediate\_value)  
example : sll 4 1 0x02

take the value in reg1 left shift it by 2 bits and store it in reg4

opcode : 0000\_1010

changes : a new module was added to the ALU and it has 24 muxes. A new ALU opcode was introduced and it is selected in the CU when necessary.  
Mux diagram is shown below.

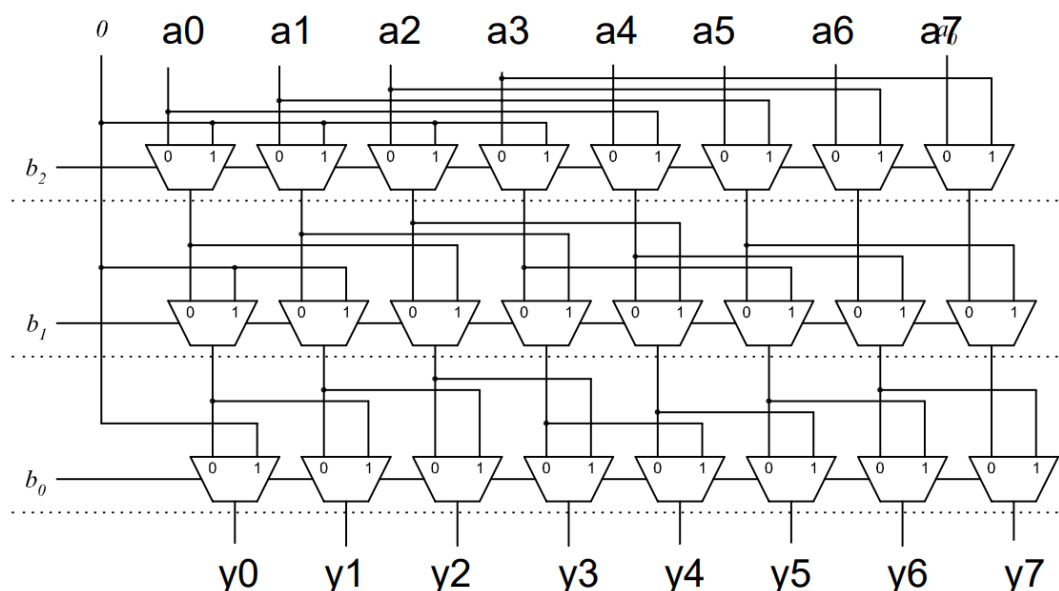Timing : to simulate the delays, 2 time units of delay was added to the new module inside ALU



8-bit Logical Left Shifter

## **sra – Arithmetic Shift Right**

This instruction right arithmetic shifts a value in a specified register by the amount specified in the immediate value, and stores in a specified register.

Instruction Structure : sra(store reg) (value taken reg) 0x(immediate\_value)  
example : sra 4 1 0x02

take the value in reg1 arithmetic right shift it by 2 bits and store it in reg4

opcode : 0000\_1011

changes : a new module was added to the ALU and it has 24 muxes. A new ALU opcode was introduced and it is selected in the CU when necessary according to the Opcode.

Timing : to simulate the delays, 2 time units of delay was added to the new module inside ALU

## ror – Rotate Right

This instruction right rotates a value in a specified register by the amount specified in the immediate value, and stores in a specified register.

Instruction Structure : ror(store reg) (value taken reg) 0x(immediate\_value)


example : ror 4 1 0x02

take the value in reg1 rotate right it by 2 bits and  
store it in reg4

opcode : 0000\_1100

changes : a new module was added to the ALU and it has 24  
muxes. A new ALU opcode was introduced and it  
is selected in the CU when necessary.  
Mux diagram is shown below.

 Timing : to simulate the delays, 2 time units of delay was  
added to the new module inside ALU



8-bit right rotator.